

Why Kirchhoff's Rules?

- Analyze → To calculate currents in the circuit
- Power dissipated by a resistor(s) in a circuit etc


Kirchhoff's Rules:

1. Junction Rule: At any junction: $\sum_{\text{juncts}} I = 0$


2. Loop Rule: The sum of potential difference across all elements around any closed loop must be zero:

$$\sum_{\text{loop}} \Delta V = 0$$

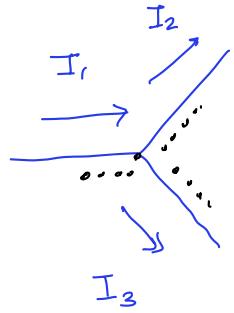1. Junction Rule: $\sum_{\text{junc}} I = 0$





$$+ I_1 - I_2 - I_3 = 0$$

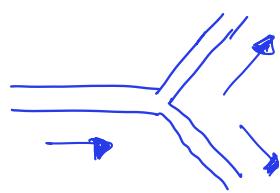


2nd Rule: Loop Rule:

$$\Delta V = V_b - V_a$$

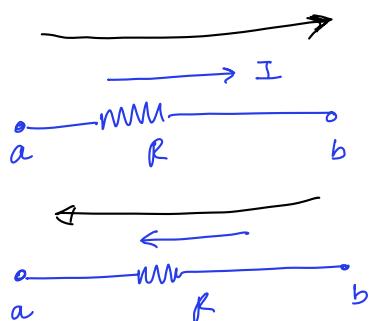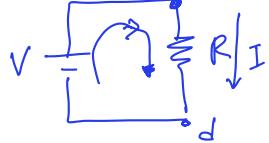

$$\Delta V = -IR$$

$$\Delta V = +IR$$

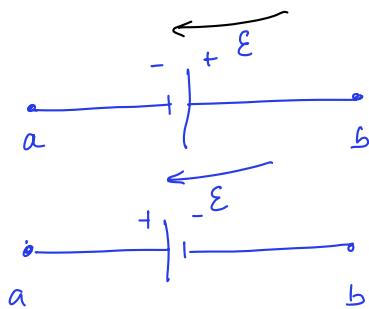

$$\Delta V = -E$$

$$\Delta V = +E$$